

## 2025 Digital IC Design Homework 1

NAME	方騏為						
Student ID	F74102250						
<b>Functional Simulation Result</b>							
Stage 1	Pass	Stage 2	Pass	Stage 3	Pass	Stage 4	Pass
<b>Stage 1</b>							
<pre> # -----          Stagel: Comparator2 Pass !          ----- # # -----          Stage2: MedianFinder_3num Pass !      ----- # # -----          Stage3: MedianFinder_5num Pass !      ----- # # -----          Stage4: MedianFinder_7num Pass !      ----- # </pre>							
<b>Stage 2</b>							
<pre> # -----          Stagel: Comparator2 Pass !          ----- # # -----          Stage2: MedianFinder_3num Pass !      ----- # # -----          Stage3: MedianFinder_5num Pass !      ----- # # -----          Stage4: MedianFinder_7num Pass !      ----- # </pre>							
<b>Stage 3</b>							
<pre> # -----          Stagel: Comparator2 Pass !          ----- # # -----          Stage2: MedianFinder_3num Pass !      ----- # # -----          Stage3: MedianFinder_5num Pass !      ----- # # -----          Stage4: MedianFinder_7num Pass !      ----- # </pre>							
<b>Stage 4</b>							
<pre> # -----          Stagel: Comparator2 Pass !          ----- # # -----          Stage2: MedianFinder_3num Pass !      ----- # # -----          Stage3: MedianFinder_5num Pass !      ----- # # -----          Stage4: MedianFinder_7num Pass !      ----- # </pre>							
<b>Description of your design</b>							
<p>前三題都按照指示的圖寫就好，最後一題先挑 6 個數字出來 然後用 comparator2 去找出三對 min ,max，再分別找出三個 min 中最小的，和三個 max 中最大的，分別淘汰掉，就剩 4 個數和沒有做過的數字，總共 5 個，放進 MedianFinder_5num 就好。</p>							